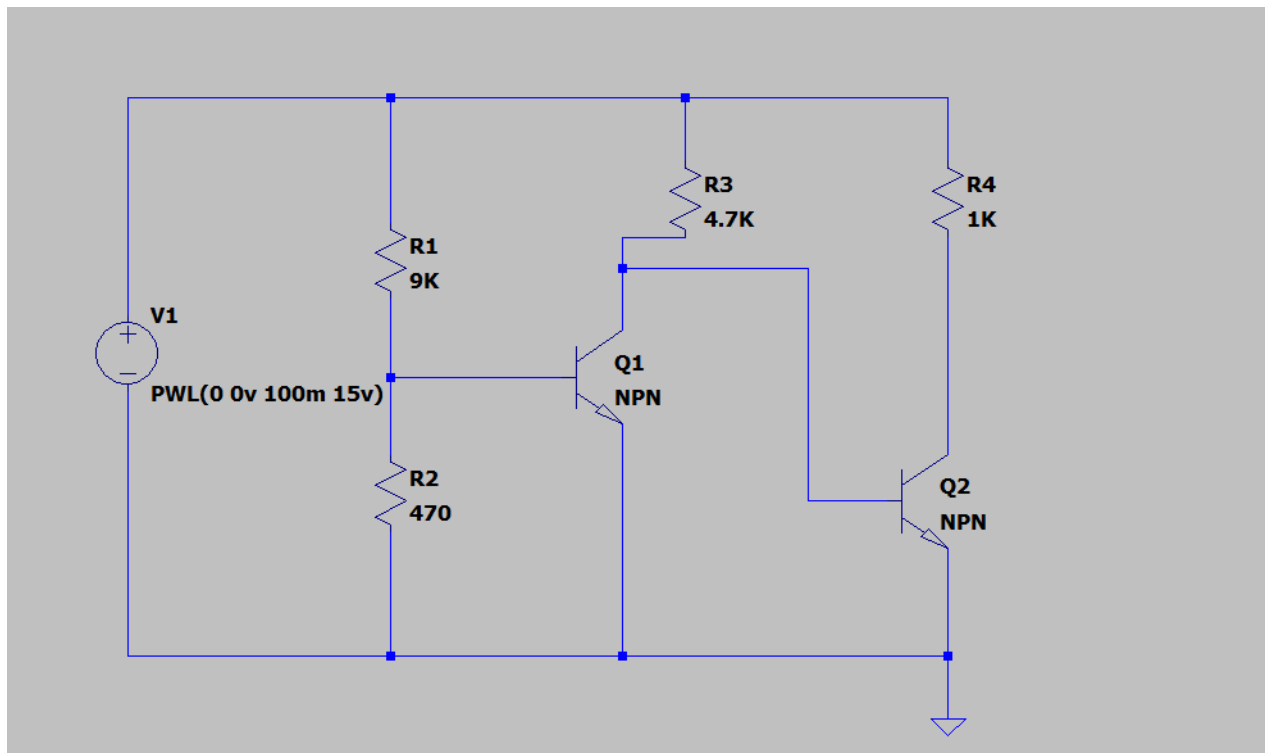


NPN BJT and PNP BJT Overvoltage Protection Circuits

NPN BJT Overvoltage Protection:

Circuit:



Circuit Design:

The circuit utilizes NPN transistors (Q1 and Q2) for switching and load protection, with resistors (R1, R2, R3, and R4) defining reference voltages and influencing transistor


behavior. A PWL voltage source simulates varying input voltages over time, ramping from 0V to 15V within 100 milliseconds to model a rising voltage scenario. Resistors R1 and R3 form a voltage divider that sets the base voltage of Q1, while R2 supplies base current to Q2. R4 serves as the load resistor. Transistor Q1 monitors the input voltage and activates when its base-emitter voltage exceeds approximately 0.6V, controlling the base of Q2. When Q1 turns on, it deactivates Q2, thereby disconnecting the load resistor R4 from the circuit. Conversely, if Q1 is off, Q2 remains active, allowing current to pass through the load.

Circuit Operation:

In normal operation, when the input voltage is below a certain threshold, the base-emitter voltage of Q1 remains below 0.6V, keeping Q1 in the off state. Consequently, Q2 is activated, allowing current to flow through the load resistor R4 and thus powering the load. As the input voltage rises and surpasses the threshold, Q1 turns on. This activation causes the collector voltage of Q1 to drop close to 0V, which, in turn, deactivates Q2. With Q2 turned off, current is prevented from flowing through R4, thereby protecting the load from excessive voltage and ensuring overvoltage conditions are managed effectively.

PNP BJT Overvoltage Protection:

Circuit:

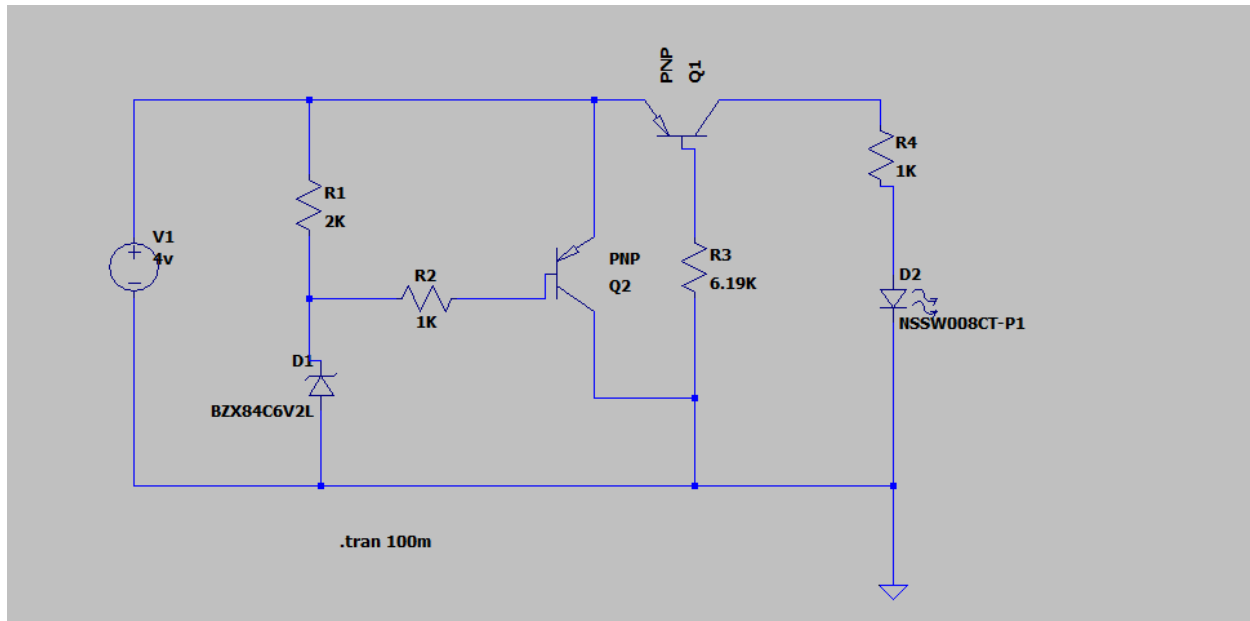

Circuit Design:

The circuit design for the simple overvoltage protection system utilizes a few easily accessible components to ensure voltage regulation and protection. The core components include a Zener diode, two PNP transistors (BC557), resistors, and an LED. The Zener diode, with a specified breakdown voltage of 5.1V, acts as the primary voltage regulator. It is chosen based on the required voltage range for the load, which in this case is 5V. The circuit incorporates two BC557 PNP transistors, which function as switches to control the flow of current based on the voltage level. Additional resistors (2K Ω , 6.2K Ω , and 1K Ω) are used to


set the appropriate biasing levels for the transistors. An LED is included to visually indicate when the output voltage is within the allowed range. The design ensures that the load is protected from overvoltage conditions by controlling the transistors' switching behavior.

Circuit Operation:

In operation, when the DC power supply is applied to the circuit, the Zener diode is reverse-biased and maintains a regulated voltage level. If the input voltage is below the preset value, the Zener diode does not conduct, and the base of the first PNP transistor (Q1) remains high. This condition keeps Q1 turned off, which in turn keeps the base of the second PNP transistor (Q2) low. As a result, Q2 is in its conducting state, allowing current to flow through the load. When the input voltage exceeds the preset value, the Zener diode begins conducting, pulling the base of Q1 to ground and turning it on. This action turns on Q2, which then acts as an open switch, blocking the current flow and protecting the load from overvoltage. The LED positioned near the output serves as an indicator, lighting up to show that the output voltage is within the safe range. This circuit is suitable for applications where voltage protection is required, such as in various electrical appliances.

Simulation Results:


NPN BJT Overvoltage Protection Result:

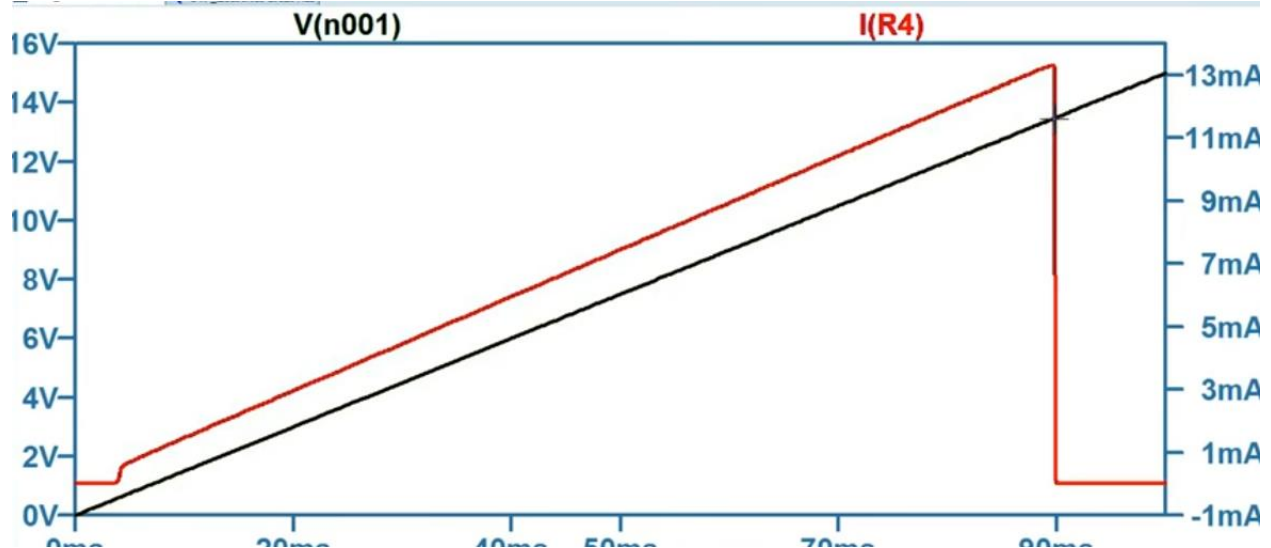

The results from the overvoltage protection circuit show that it effectively protects the load from high voltage. When the input voltage is below the set threshold, the Zener diode does not conduct electricity, keeping the base of the first PNP transistor (Q1) high. This keeps Q1 turned off, allowing the second PNP transistor (Q2) to stay on and let current flow through the load resistor, which powers the load as expected. When the input voltage rises above the threshold, the Zener diode starts conducting, which pulls the base of Q1 down to ground and turns it on. This action turns off Q2, stopping the current flow through the load resistor as shown in the simulation and protecting the load from the high voltage. Overall, the circuit successfully switches between

normal operation and protective mode based on the input voltage, ensuring that voltage-sensitive components are protected, and electrical appliances operate safely.

PNP BJT Overvoltage Protection Result:

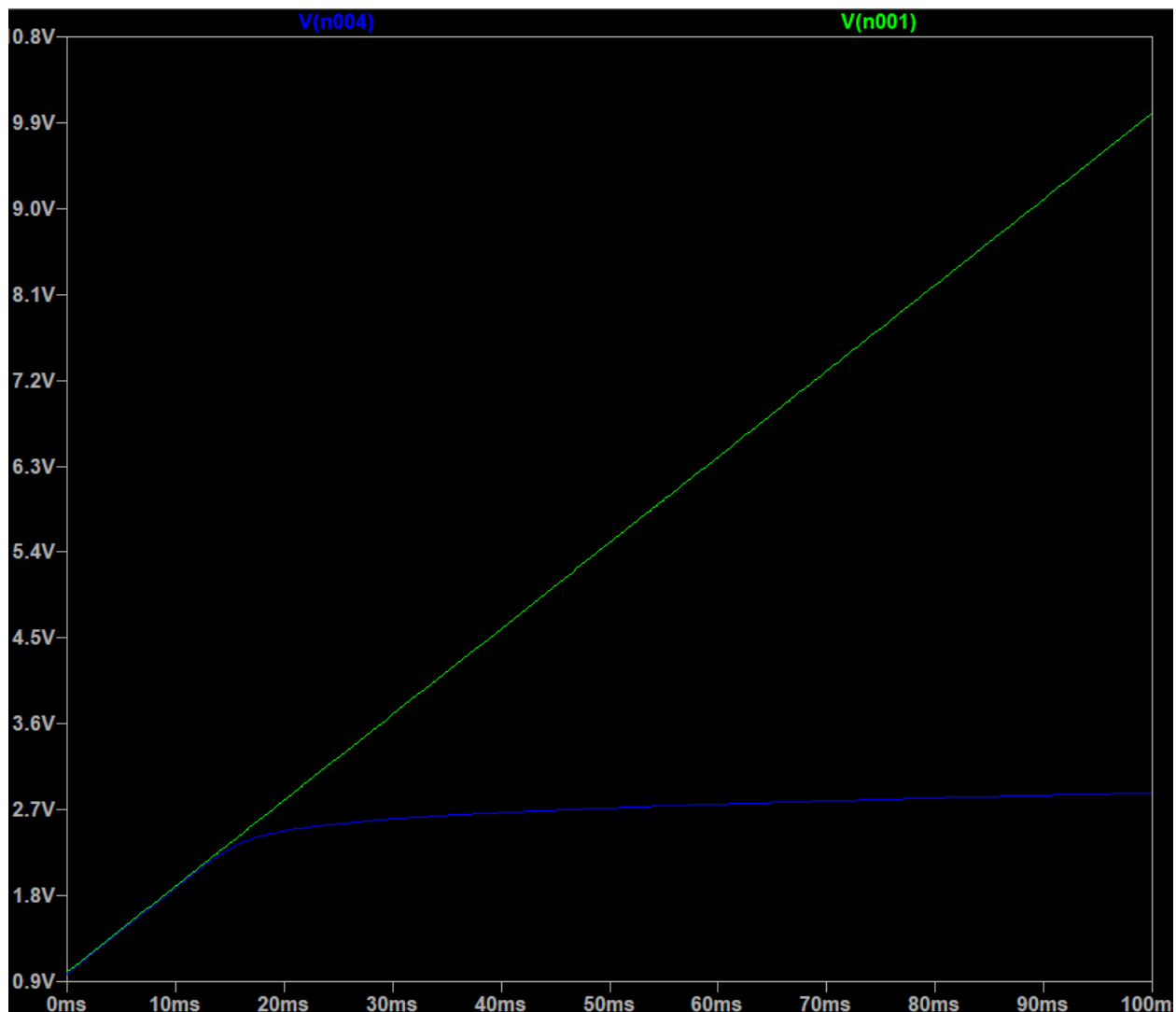

The results of the PNP transistor-based overvoltage protection circuit show that it works well to protect the load from too much voltage. When the input voltage is below the

safe level set by the Zener diode, the diode does not conduct, which keeps the first PNP transistor (Q1) turned off. This lets the second PNP transistor (Q2) stay on, allowing current to flow through the load resistor and power the load as needed.

However, when the input voltage rises above the safe level, the Zener diode starts to conduct. This pulls the base of Q1 down to ground, turning Q1 on. As a result, Q2 is turned off, stopping the current from flowing through the load resistor and protecting the load from too much voltage.

The LED in the circuit lights up when the voltage is at a safe level, showing that the load is getting power. If the LED goes out, it means the voltage is too high, and the circuit has stopped the current to protect the load.

In summary, the PNP transistor circuit successfully switches between powering the load and protecting it from overvoltage. The LED indicator provides an easy way to see if the voltage is safe or if the circuit is protecting the load.

Comparison and Differences:

1. Transistor Types:

- **NPN Circuit:** Uses NPN transistors. NPN transistors are active when a positive voltage is applied to the base relative to the emitter.
- **PNP Circuit:** Uses PNP transistors. PNP transistors are active when a negative voltage is applied to the base relative to the emitter.

2. Triggering Mechanism

- **NPN Circuit:** The NPN circuit uses a voltage divider and the base-emitter voltage to control the transistors. When the input voltage exceeds the set threshold, Q1 turns on, causing Q2 to turn off.
- **PNP Circuit:** The PNP circuit uses a Zener diode to regulate voltage. When the input voltage is too high, the Zener diode conducts, turning Q1 on, which in turn turns Q2 off.

3. Operation of Protection:

- **NPN Circuit:** The NPN circuit relies on the voltage drop across resistors to manage the switching of transistors. The load is disconnected by turning off Q2 when the input voltage is too high.
- **PNP Circuit:** The PNP circuit uses a Zener diode to directly control the base of Q1. The load is disconnected by turning off Q2 when the Zener diode conducts due to overvoltage.

Conclusion:

In summary, both circuits aim to protect a load from overvoltage, but they use different types of transistors and methods to achieve this. The NPN circuit relies on a voltage divider and transistor switching, while the PNP circuit uses a Zener diode to regulate voltage and control the transistors. The choice between these circuits depends on the specific requirements of the application, including the type of transistors used and the desired method for setting the voltage threshold.